

**Marko Markovic, VHDL SPR MAG, Kol I**

## **DIO A , ZADATAK 12**

### **KOD:**

-- BCD to 7 segment counter

library ieee;

use ieee.std\_logic\_1164.all;

entity bcdto7seg is

port

(

    bcd: in std\_logic\_vector(3 downto 0);

    seg: out std\_logic\_vector(6 downto 0)

);

end bcdto7seg;

architecture arh\_bcdto7seg of bcdto7seg is

begin

    with bcd select

    seg<= "1111110" when "0000",

        "0110000" when "0001",

        "1101101" when "0010",

        "1111001" when "0011",

        "0110011" when "0100",


        "1011011" when "0101",

        "1011111" when "0110",


"1110000" when "0111",  
 "1111111" when "1000",  
 "1110011" when "1001",  
 "1110111" when "1010",  
 "0011111" when "1011",  
 "1001110" when "1100",  
 "0111101" when "1101",  
 "1001111" when "1110",  
 "1000111" when "1111";

end arh\_bcdto7seg;

## SIMULACIJA:

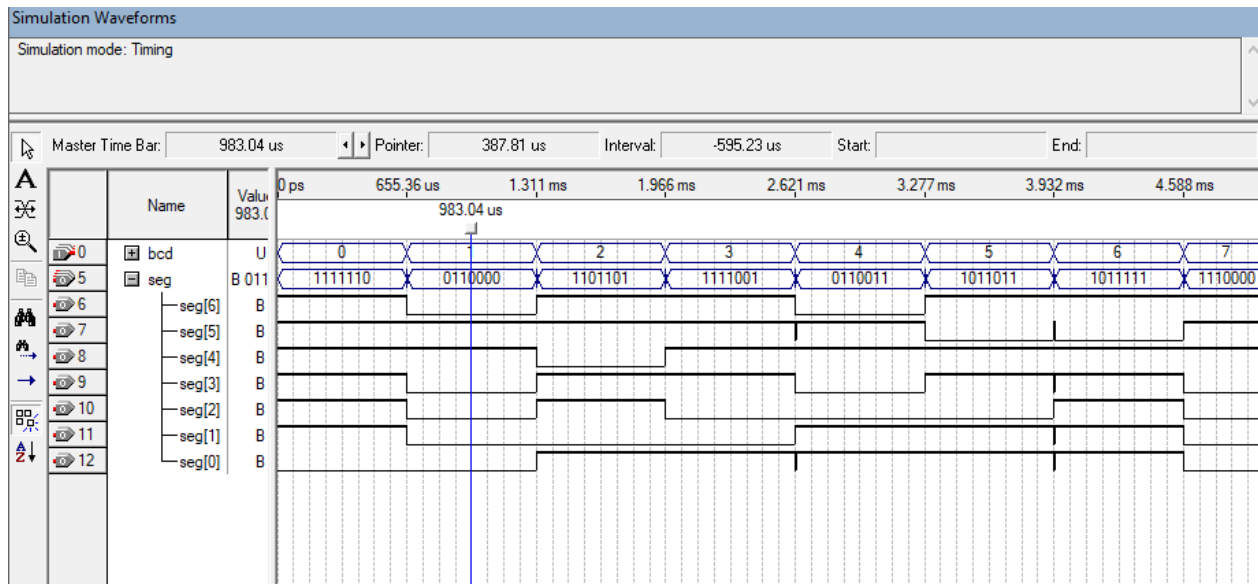

 **Za bcd="1" DEC, seg="0110000", BINARY, gdje se seg[6]=MSB**



## DIO B, ZADATAK 3

### KOD:

-- 4 bits up counter

library ieee ;

use ieee.std\_logic\_1164.all;

use ieee.std\_logic\_unsigned.all;

entity four\_up\_counter is

generic (N: natural :=3);

port

(

clock: in std\_logic;

clear: in std\_logic;

enable: in std\_logic;

Q: out std\_logic\_vector (N downto 0)

);

end four\_up\_counter;

architecture arh\_of\_counter of four\_up\_counter is

```

signal temp: std_logic_vector (N downto 0);

begin

process (clock, clear, enable)

begin

if clear = '1' then

temp <= temp - temp;

elsif (falling_edge (clock)) then

if enable = '1' then

temp <= temp + 1;

end if;

end if;


end process;

Q <= temp;

end arh_of_counter;

```

## SIMULACIJA

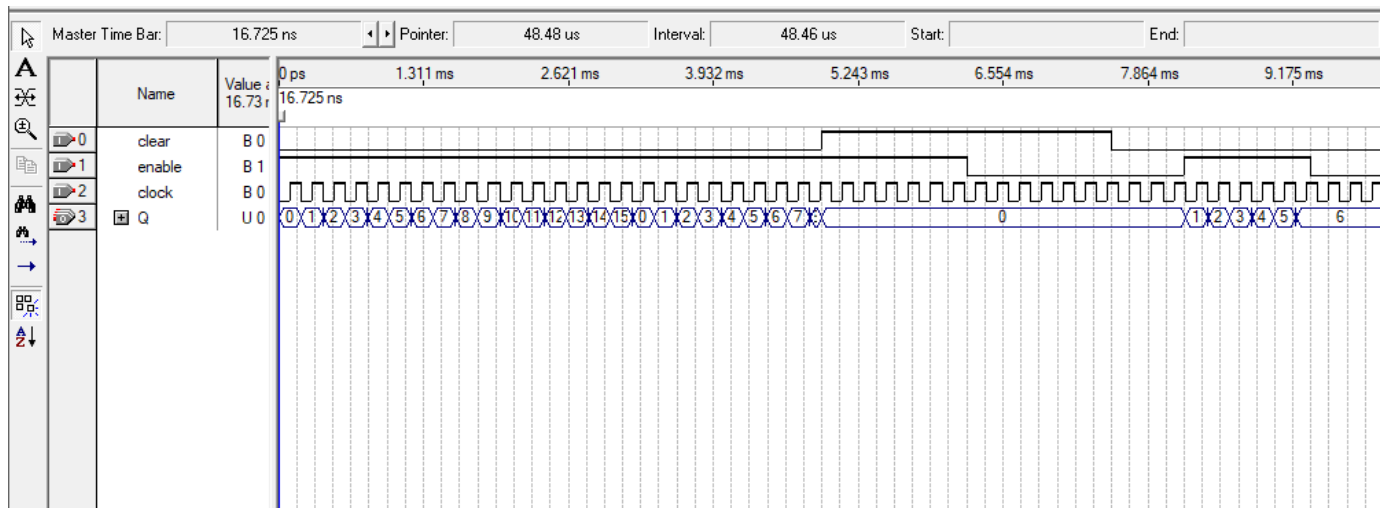

**Kada je clear=0, enable=1, tada Q broji od 0-15-0-15. Kada je clear=1, bez obzira sta je enable, tada ke Q=0. Kada clear=0,**

**enable=1, pa potom 0, tada brojac zadržava zadnju vrijednost, u našem slučaju 6.**