 


VHDL, Lab1, Vježbe, 2018

A) Kombinaciona kola

1. Za kolo prikazano na slici 1. napisati VHDL kod. Priložiti kod i simulacione dijagrame.




Slika 1.

2. Za kolo polu-sabirača :
 - a) Napisati VHDL kod.
 - b) Kreirati simbol.
 - c) Koristeći simbol polu-sabirača i logičko kolo XOR u grafičkom editoru projektovati puni sabirač.
 - d) Simulacijom verifikovati ispravnost dizajna punog sabirača. Parametre *End Time* i *Grid Size* postaviti na vrijednosti $2\mu\text{s}$ i 200ns , respektivno.
3. a) Projektovati kolo u VHDLu 4-to-1 1-bit MUXa.

| IO Pins | Description |
|------------|--------------|
| a, b, c, d | Data Inputs |
| s[1:0] | MUX selector |
| o | Data Output |


b) Koristeći kreirani symbol Mux-a 4-1 i Mux 2-1, projektovati kolo multipleksora 8-1 i simulirati njegov rad.

 7. Konstruisati BCD-SEDMOSEGMENTNI dekođer. Displej može prikazivati i brojeve (0 do 9) i slova (A, B, C, D, E i F). Displej je aktivan logičkom 1. Prikazati rezultat simulacije za BCD="0111". Priložiti kod i simulacioni dijagram.



B) SEKVENCIJALNA KOLA

 5. a) Projektovati u VHDL-u D Flip Flop sa ENABLE ulazom i klokom na pozitivnoj ivici
- b) Formirati simbol.
- c) Koristeći simbol DFF i inverter u grafičkom editoru napravite djeliteelj frekvencije kloka sa 2.



6. Projektovati RS flip flop sa clear i set ulazima. Uočiti detla delay. Priložiti kod i simulacione dijagrame.
7. Donja tabela prikazuje definiciju pinova N bitnog brojača sa asinhronim clearom. Priložiti VHDL kod i simulacione dijagrame. Dizajnirati kod i sprovesti simulaciju.

| IO Pins | Description |
|---------|---------------------|
| clock | Positive-Edge Clock |

| | |
|--------|----------------------------------|
| clear | Asynchronous Clear (active High) |
| enable | Enable input (active High) |
| Q[N:0] | Data Output |

Pomoc:

```

library ieee ;
use ieee.std_logic_1164.all;
use ieee.std_logic_unsigned.all;

-----

entity counter is

generic(N: natural :=2);
port(  clock: in std_logic;
      clear: in std_logic;
      enable: in std_logic;
      Q:      out std_logic_vector(N-1 downto 0)
);
end counter;

-----

architecture behv of counter is

    signal Pre_Q: std_logic_vector(N-1 downto 0);

begin

    -- princip rada opis

    process(clock, count, clear)
    begin
        if clear = '1' then
            Pre_Q <= Pre_Q - Pre_Q;
        elsif (clock='1' and clock'event) then
            if enable = '1' then
                Pre_Q <= Pre_Q + 1; -- reset
            end if;
        end if;
    end process;

    -- concurrent assignment statement
    Q <= Pre_Q;

end behv;

```

8. Projektovati kolo Nbitnog UP/DOWN brojača u VHDLu. Osnova brojanja se određuje generičkom konstantom N. Brojač posjeduje CLR ulaz koji su aktivni sa logičkom „0”, a signa; direkcije DIR="1". Priložiti kod i simulacione dijagrame, fclk=1ms.

| IO Pins | Description |
|---------|-------------------------------------|
| C | Positive-Edge Clock |
| CLR | Asynchronous Clear (active High) |
| UP_DOWN | up/down count mode selector |
| Q[3:0] | Data Output |

Napomena:

Dolaze 2 zadatka, po jedan iz gornjih oblasti (A,B).

Zadaci se rade prema datom templateu i Primjerima datim na sajtu. Predaju se na casu u vidu doc dokumenta.

Ako se zeli odlaganje termina , to uraditi preko predstavnika

Podgorica 13. 03. 2018